
 


Homework: the following circuit and timing diagrams illustrate the differences between D-latch, rising edge triggered D flip-flop, falling edge triggered D flip-flop, T flip-flop, and JK flip-flop (the input K hardwired to 1). Write Verilog design codes and a testbench to reproduce the following waveforms. You need to initialize Q to 0 at the declaration (e.g. reg Q = 0;) for each flip-flop module. You can test all the flip-flops at once in one testbench.

 

```

testbench.sv
// Gianna Rose
// Lab 10 HW
// https://www.edaplayground.com/x/7uAZ

module testAll;
// Clock and D inputs
reg Clock, D;
// Qa-Qe are the outputs
wire Qa, Qb, Qc, Qd, Qe;

// instantiate the UUT
differences uut(D, Clock, Qa, Qb, Qc, Qd, Qe);

// generate the clock signal
initial
begin
    Clock = 0;
    forever #5 Clock = ~Clock;
    #200 $finish;
end

initial
begin
    $dumpfile("dump.vcd");
    $dumpvars(1, testAll);

    D=0;
    #4 D=1;
    #2 D=0;
    #1 D=1;
    #1 D=0;
    #3 D=1;
    #1 D=0;
    #1 D=1;
    #1 D=0;
    #2 D=1;
    #1 D=0;
    #2 D=1;
    #2 D=0;
    #10 $finish;
end

```

```
end
endmodule
```

```
design.sv
// Gianna Rose
// Lab 10 HW
// https://www.edaplayground.com/x/7uAZ

module differences(D,Clock,Qa,Qb,Qc,Qd, Qe);

// input data and clock
input D, Clock;

// output registers
output reg Qa = 0,Qb = 0,Qc = 0,Qd = 0,Qe = 0;

// JK FF
reg K = 1;
initial
    Qd <= 0;

//D-Latch
always@(*)
    if(Clock)
        Qa <= D;


    always @ (posedge Clock)
begin
    // rising edge triggered d flip flop
    Qb <= D;
    if(D)
        // t flip flop
        Qd <= ~Qd;
end

    // falling edge triggered d flip flop
    always@(negedge Clock)
    Qc <= D;

    // JK FF
    always@(posedge Clock)
        Qe <= (D & ~Qd) | (~K & Qd);

endmodule
```

Output

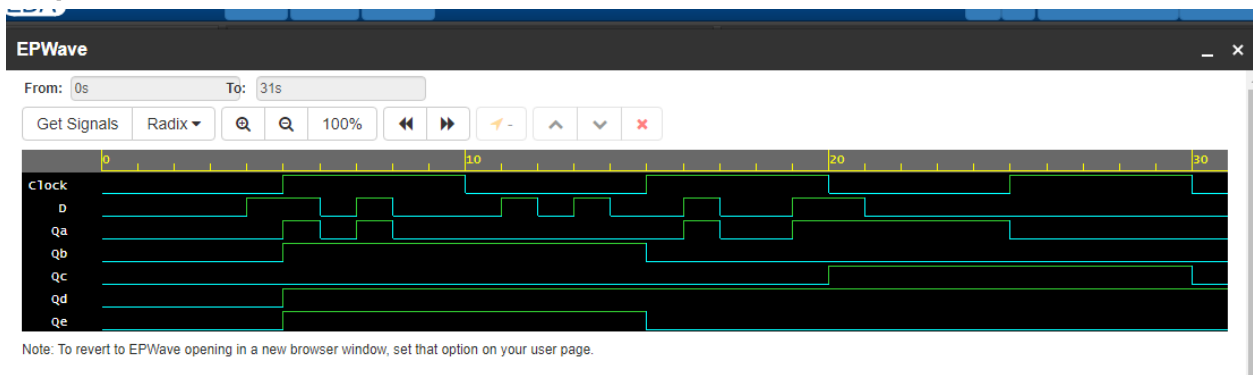

<https://www.edaplayground.com/x/7uAZ>